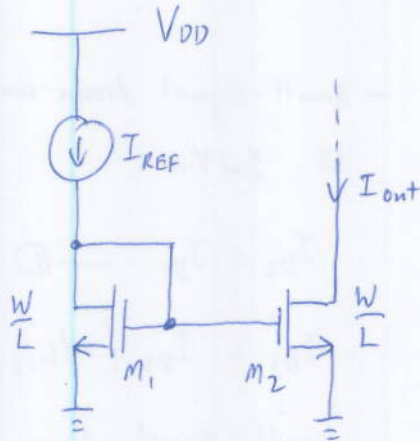


## Chapter 4 - Current Mirrors



$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 \quad \text{--- (1)}$$


$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2 \quad \text{--- (2)}$$

$$\textcircled{2} \div \textcircled{1}$$

$$I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

(E.g.)

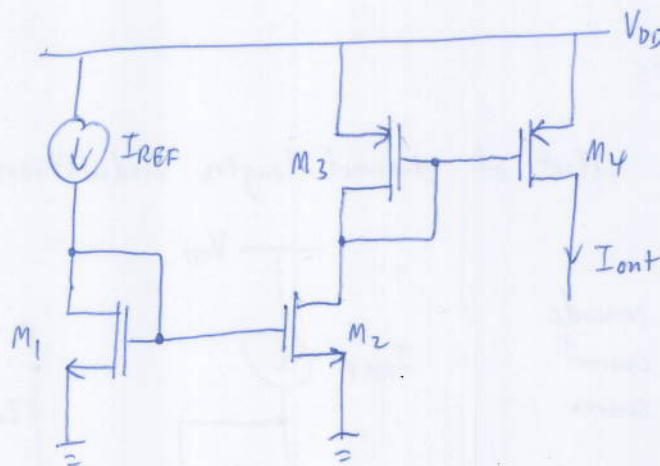Find the drain current of  $M_4$  if all of the transistors are in saturation.



Solution

$$I_{D2} = I_{REF} \left[ (W/L)_2 / (W/L)_1 \right] \quad \text{--- (1)}$$

$$|I_{D3}| = |I_{D2}| \quad \text{--- (2)}$$


$$I_{D4} = I_{D3} \left[ (W/L)_4 / (W/L)_3 \right] \quad \text{--- (3)}$$

Thus,  $|I_{D4}| = \alpha \beta I_{REF}$  where  $\alpha = (W/L)_2 / (W/L)_1$

$$\beta = (W/L)_4 / (W/L)_3$$

E.g.

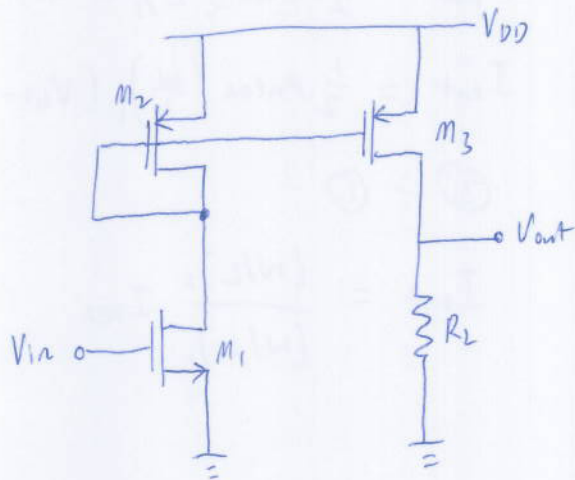Calculate the small-signal voltage gain of the circuit below



— small-signal drain current of  $M_1$  is  $g_{m1} V_{in}$ .

$$I_{D2} = I_{D1} \quad \text{--- (1)}$$


$$I_{D3} = I_{D2} (W/L)_3 / (W/L)_2 \quad \text{--- (2)}$$

— small-signal drain current of  $M_3$  is  $g_{m1} V_{in} (W/L)_3 / (W/L)_2$

$$\text{Voltage gain} = g_{m1} R_L (W/L)_3 / (W/L)_2$$
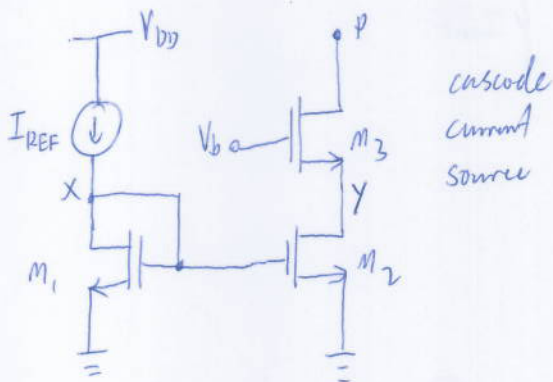
### Cascode current mirrors

→ can suppress the effect of channel-length modulation.




cascode  
current  
source

We want  $V_X = V_Y$ ,

$$V_b - V_{GS3} = V_X$$

$$V_b = V_X + V_{GS3}$$

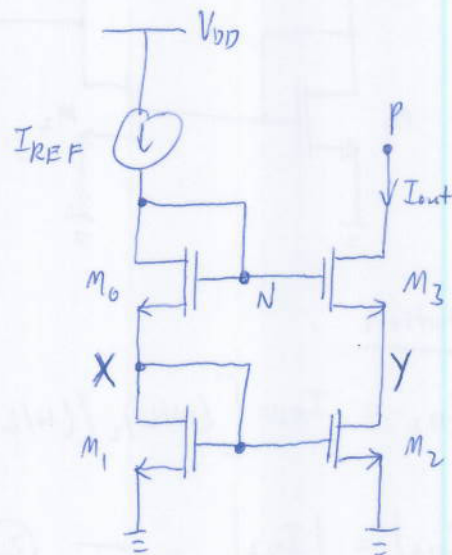

cascode  
current  
mirror

$$V_N = V_{GS0} + V_X = V_{GS3} + V_Y$$


$$\text{If } (W/L)_3 / (W/L)_0 = (W/L)_2 / (W/L)_1,$$

$$V_{GS3} = V_{GS0} \quad \text{and} \quad V_X = V_Y$$

This result holds even if  $M_0$  and  $M_3$  suffer from body effect.

(E.g.)

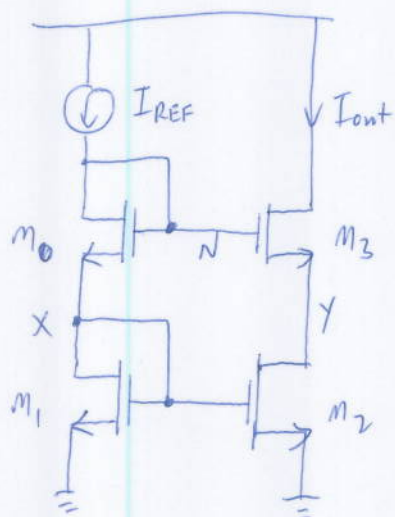If  $I_{REF}$  requires 0.5V to operate as a current source, what is its maximum value?



$M_2$  and  $M_3$  properly ratioed with respect to  $M_1$  and  $M_0$ , we have

$$V_Y = V_X \approx \sqrt{2I_{REF} / [M_n C_{ox} (W/L)_1]} + V_{TH1}$$

To find max value of  $I_{REF}$ , we note that

$$\begin{aligned} V_N &= V_{GS0} + V_{GS1} \\ &= \sqrt{\frac{2I_{REF}}{M_n C_{ox}}} \left[ \sqrt{\left(\frac{L}{W}\right)_0} + \sqrt{\left(\frac{L}{W}\right)_1} \right] + V_{TH0} + V_{TH1} \end{aligned}$$

Thus,

$$V_{DD} - \sqrt{\frac{2I_{REF}}{M_n C_{ox}}} \left[ \sqrt{\left(\frac{L}{W}\right)_0} + \sqrt{\left(\frac{L}{W}\right)_1} \right] - V_{TH0} - V_{TH1} = 0.5V$$



and hence,

$$I_{REF, \max} = \frac{M_n C_{ox}}{2} \frac{(V_{DD} - 0.5V - V_{TH0} - V_{TH1})^2}{(\sqrt{(L/W)_0} + \sqrt{(L/W)_1})^2}$$



## Active Current Mirrors

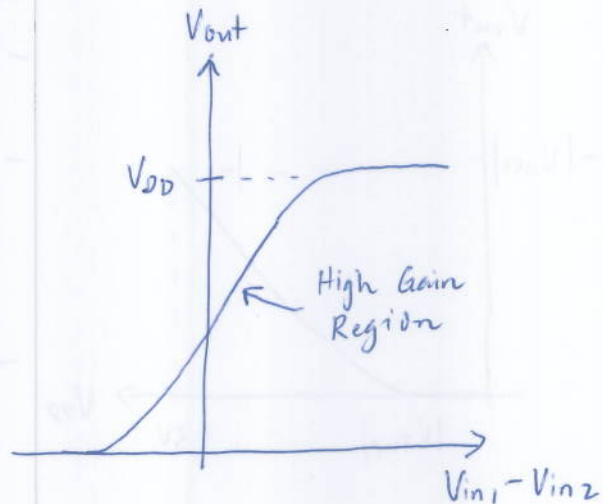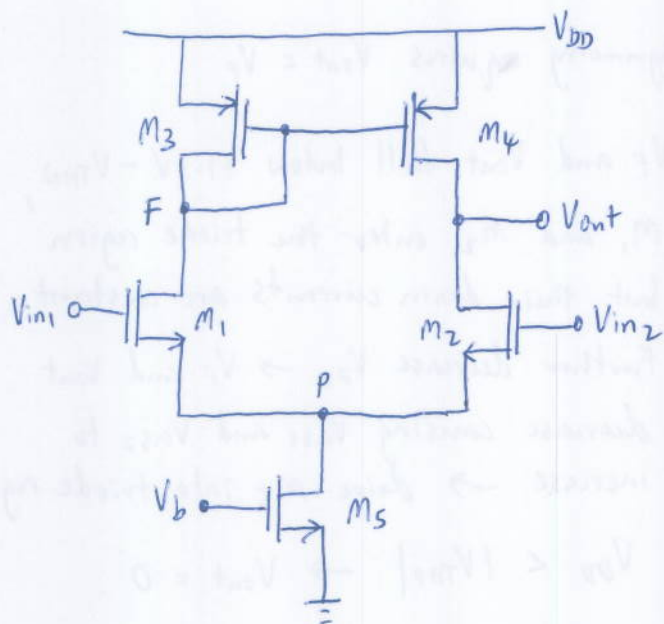
### Differential pair with active current mirror



- If  $V_{in1}$  much more negative than  $V_{in2}$ ,  $M_1$ ,  $M_3$  and  $M_4$  are off
- No current can flow from  $V_{DD}$   $\rightarrow$   $M_2$  and  $M_5$  operate in deep triode region, carrying zero current.  
 $\rightarrow V_{out} = 0$
- If  $V_{in1}$  approaches  $V_{in2}$ ,  $M_1$  turns on, drawing part of  $I_{D5}$  from  $M_3$  and turning on  $M_4$
- The output voltage then depends on the difference between  $I_{D4}$  and  $I_{D2}$
- Small difference between  $V_{in1}$  and  $V_{in2}$ , both  $M_2$  and  $M_4$  are saturated  
 $\rightarrow$  provides a high gain.
- As  $V_{in1}$  becomes more positive than  $V_{in2}$ ,  $I_{D1}$ ,  $|I_{D3}|$ , and  $|I_{D4}|$  increase and  $I_{D2}$  decreases, driving  $M_4$  into the triode region.
- If  $V_{in1} - V_{in2}$  is sufficiently large,  $M_2$  turns off,  $M_4$  operates in deep triode region with zero current, and  $V_{out} = V_{DD}$
- Note that if  $V_{in1} > V_F + V_{TH}$ , then  $M_1$  enters the triode region.




(E.g.)

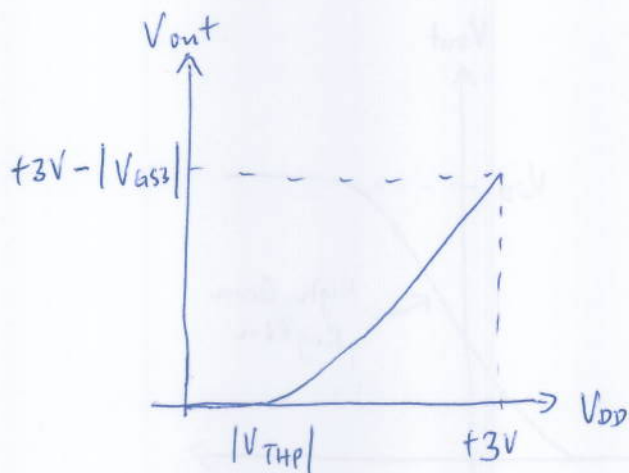Based on previous figures, if  $V_{in1} = V_{in2} = +1.5V$ , sketch the output voltage of the circuit as  $V_{DD}$  varies from  $3V$  to zero. Assume that for  $V_{DD} = 3V$  all of the devices are saturated.



- Symmetry requires  $V_{out} = V_F$
- $V_F$  and  $V_{out}$  fall below  $+1.5V - V_{THN}$ ,  $M_1$  and  $M_2$  enter the triode region but their drain currents are constant.
- Further decrease  $V_{DD} \rightarrow V_F$  and  $V_{out}$  decrease causing  $V_{GS1}$  and  $V_{GS2}$  to increase  $\rightarrow$  drive  $M_5$  into triode region
- $V_{DD} < |V_{THP}| \rightarrow V_{out} = 0$ .

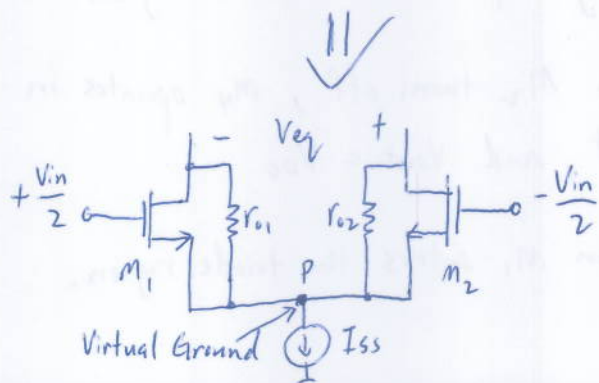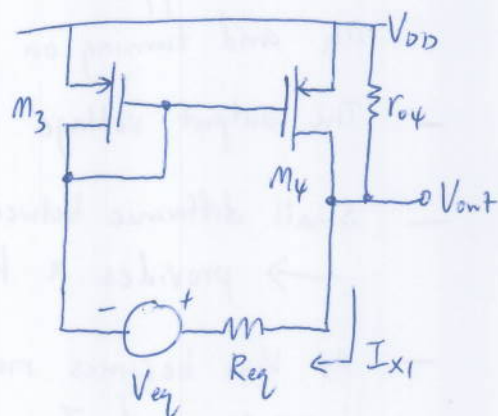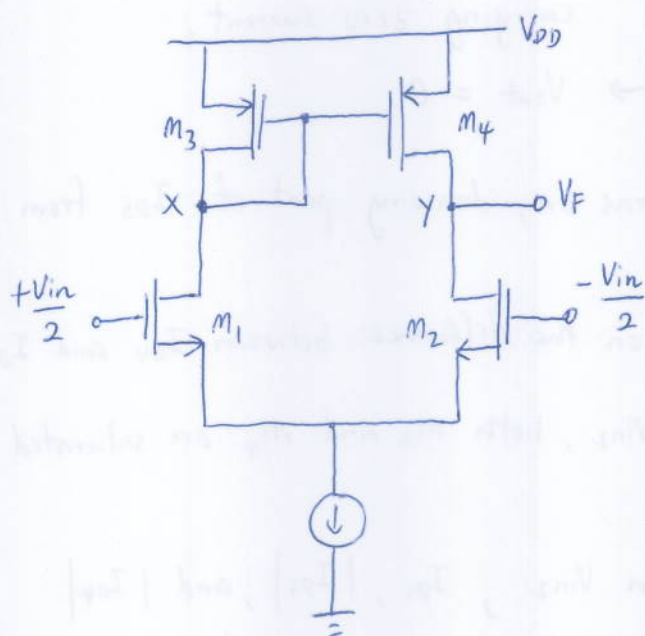Using Thevenin Equivalent to find small signal gain



Current through  $R_{eq}$ ,

$$I_{x1} = \frac{V_{out} - V_{eq}}{R_{eq} + R_{M3}} \\ = \frac{V_{out} - g_{m1,2} r_{o1,2} V_{in}}{2r_{o1,2} + \frac{1}{g_{m3}} \parallel r_{o3}}$$

$I_{1/g_{m3}}$

The fraction of this current is mirrored into  $M_4$  with unity gain,

$$2 \frac{V_{out} - g_{m1,2} r_{o1,2} V_{in}}{2r_{o1,2} + \frac{1}{g_{m3}} \parallel r_{o3}} \cdot \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} = - \frac{V_{out}}{r_{o4}}$$

Assuming  $2r_{o1,2} \gg \frac{1}{g_{m3,4}} \parallel r_{o3,4}$ , the voltage gain is

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1,2} r_{o3,4} r_{o1,2}}{r_{o1,2} + r_{o3,4}} = g_{m1,2} (r_{o1,2} \parallel r_{o3,4})$$