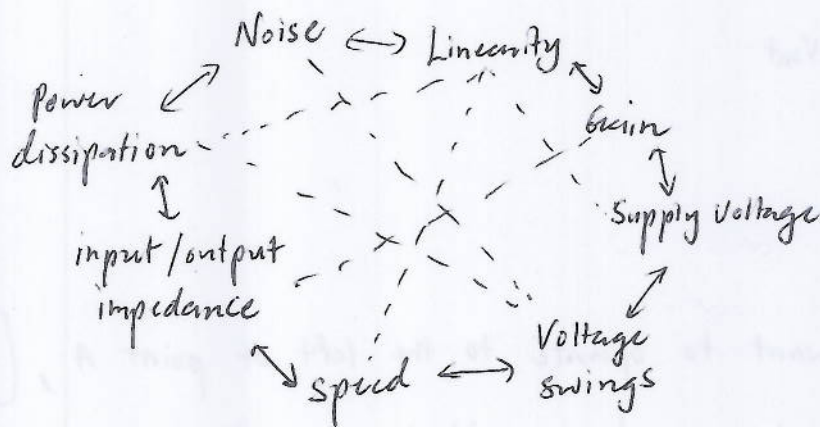





Chapter 2 - Single-Stage Amplifiers

Basic concepts



Common - Source Stage

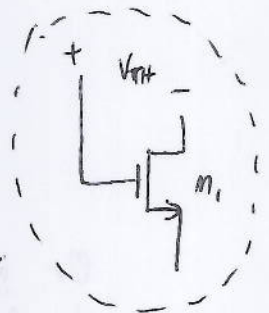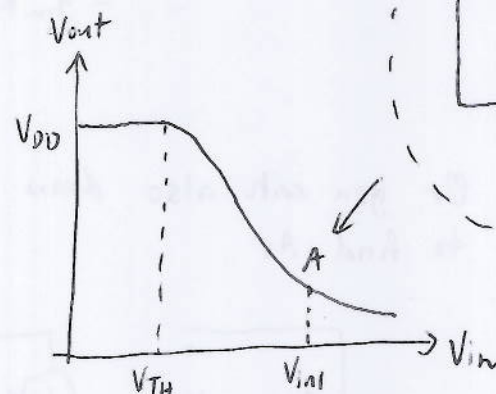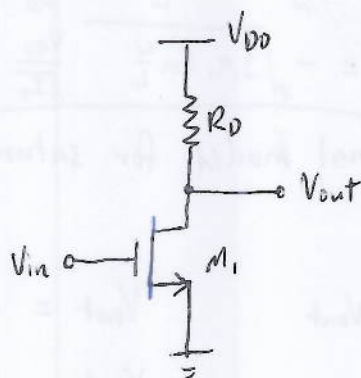(A) Common-Source stage with Resistive Load.



If M_1 in saturation,

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$


At point A,

$$V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

For $V_{in} > V_{in1}$, M_1 in triode region

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{in} - V_{TH})V_{out} - V_{out}^2]$$

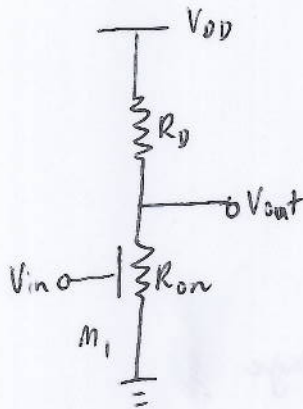If V_{in} is high enough, M_1 is in deep triode region, $V_{out} \ll 2(V_{in} - V_{TH})$



$$V_{out} = V_{DD} \frac{R_{on}}{R_{on} + R_D} = \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})}$$

Normally we want to operate to the left of point A, $[V_{out} > V_{in} - V_{TH}]$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$


$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$= -g_m R_D$$

$$A_v = -\sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \frac{V_{RD}}{I_D}$$

$$= -\sqrt{2 \mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$


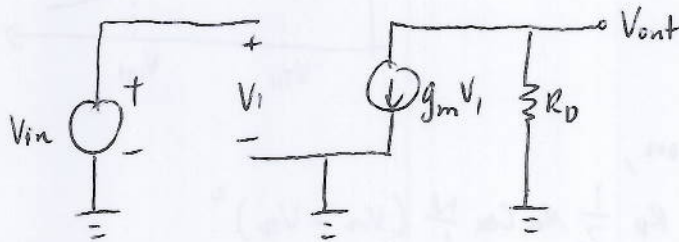
Or you can also draw small-signal model for saturation region. to find A_v



$$V_{out} = -g_m V_{in} \times R_D$$

$$A_v = \frac{V_{out}}{V_{in}} = -g_m R_D$$

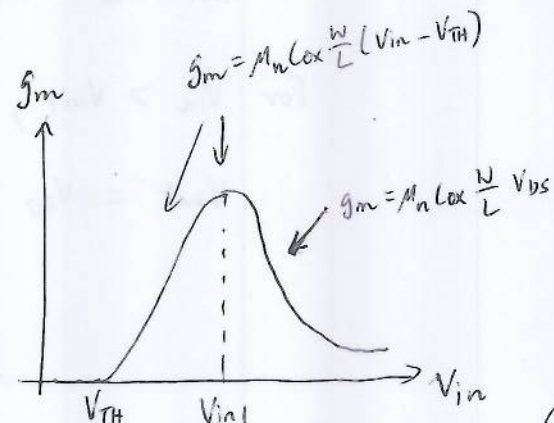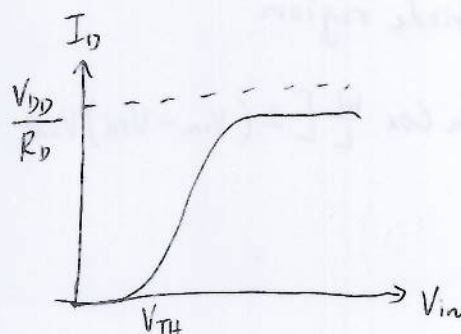(E.g.) Sketch the drain current and transconductance of M_1 as a function of the input voltage.



Effect of channel length modulation.

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$


$$\text{Using } I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2, \quad g_m = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$A_v = -R_D g_m - R_D I_D \lambda A_v$$

$$= - \frac{g_m R_D}{1 + R_D \lambda I_D}$$

$$\text{Since } \lambda I_D = \frac{1}{r_o}, \quad A_v = -g_m \frac{r_o R_D}{r_o + R_D}$$

Or use small-signal model to find A_v ,

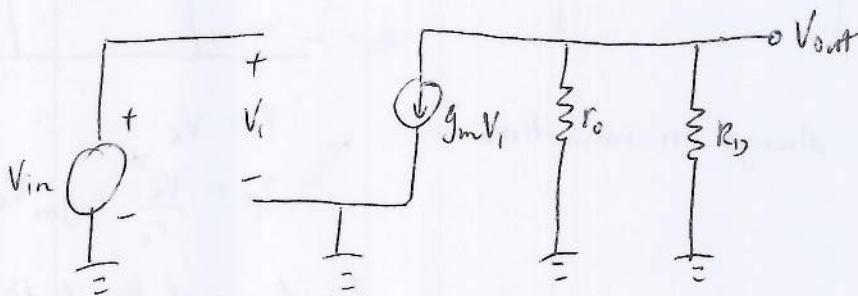


$$V_{out} = -g_m V_i (r_o \parallel R_D), \quad V_i = V_{in}$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_D)$$

(E.g.)

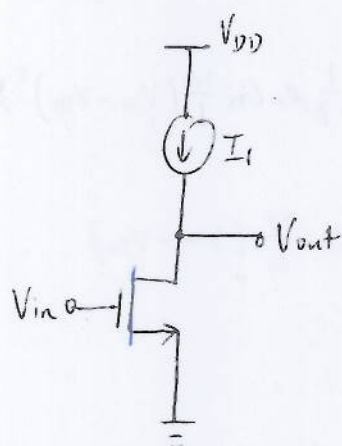Assuming M_1 is biased in saturation, calculate the small-signal voltage gain of the circuit.






I_1 introduce infinite impedance,

\therefore gain limited by output resistance of M_1 .

$$A_v = -g_m r_o$$

(B)

CS Stage with Diode-Connected Load.

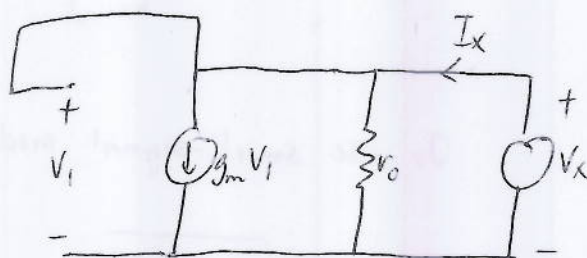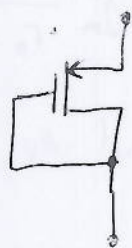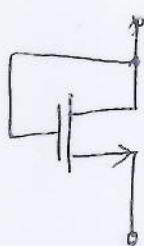

Transistor always in saturation mode.



$$V_i = V_x$$

$$I_x = \frac{V_x}{r_o} + g_m V_x$$

Impedance of the diode,

$$\left(\frac{1}{g_m} \right) \parallel r_o \approx \frac{1}{g_m}$$

If body effect exist,

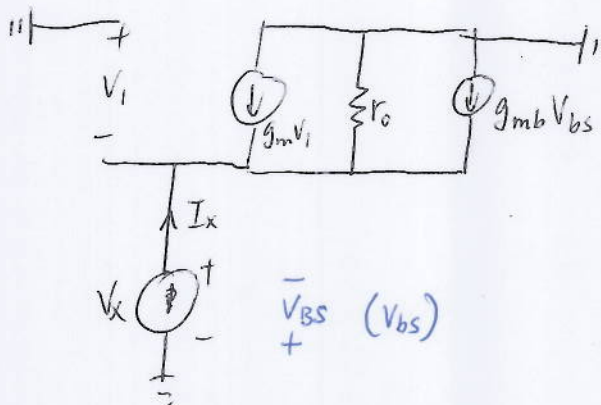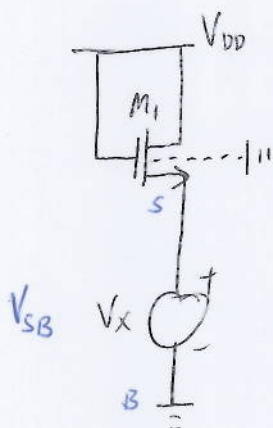


$$V_1 = -V_x, \quad V_{bs} = -V_x$$

$$V_1 = -V_{bs}, \quad V_{bs} = -V_{bs}$$

$$(g_m + g_{mb}) V_x + \frac{V_x}{r_o} = I_x$$

$$\frac{V_x}{I_x} = \frac{1}{g_m + g_{mb} + r_o^{-1}}$$
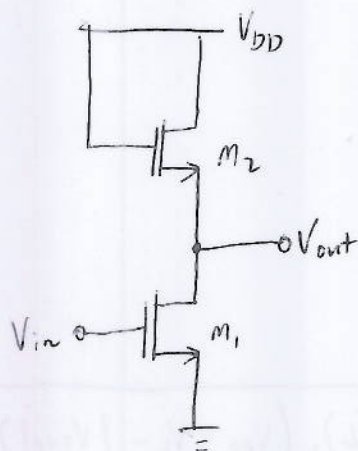
$$= \left(\frac{1}{g_m + g_{mb}} \right) \parallel r_o \approx \frac{1}{g_m + g_{mb}}$$



$$\lambda = 0, \quad \gamma \neq 0$$

$$A_v = -g_{m1} \left(\frac{1}{g_{m2} + g_{mb2}} \right)$$

$$= -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \mu}$$

$$\mu = \frac{g_{mb2}}{g_{m2}}$$

$$= -\frac{\sqrt{2\mu_n C_{ox} (W/L)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} (W/L)_2 I_{D2}}} \frac{1}{1 + \mu}$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \mu}$$


If channel-length modulation,

$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} \right)$$

If M_2 is PMOS, and no body-effect,

$$A_v = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}}$$

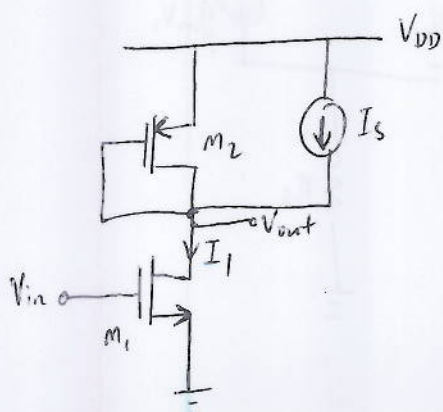E.g. M_1 is biased in saturation with a drain current equal to I_1 . The current source $I_s = 0.75 I_1$ is added to the circuit. What is the gain?




$$|I_{D2}| = I_1 / 4$$

$$\therefore A_v \approx -\frac{g_{m1}}{g_{m2}}$$

$$= -\sqrt{\frac{4\mu_n (W/L)_1}{\mu_p (W/L)_2}}$$


(C.) CS Stage with Current-Source Load

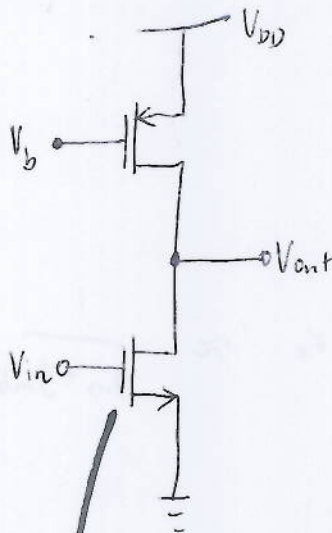

$$\lambda \neq 0, \gamma = 0$$

$$A_v = -g_{m1} (r_{o1} \parallel r_{o2})$$

(D.) CS Stage with Triode Load.


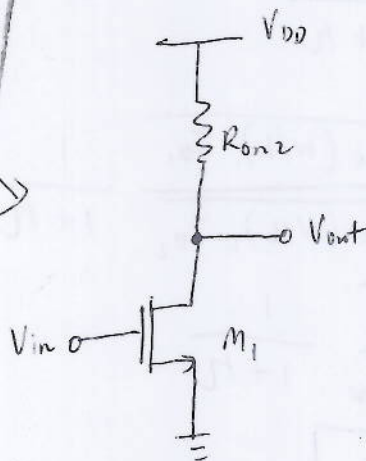


$$\lambda \neq 0, \gamma = 0$$

$$r_{on2} = \frac{1}{\mu_p C_{ox} (W/L)_2 (V_{DD} - V_b - |V_{THP}|)}$$

$$A_v = -g_{m1} (r_{o1} \parallel r_{on2})$$

(E.) CS Stage with Source Degeneration

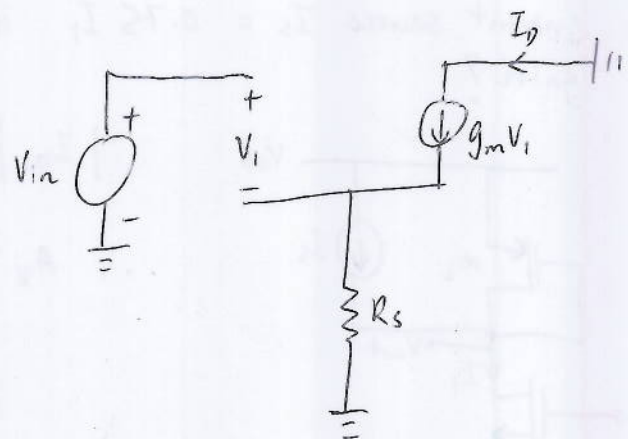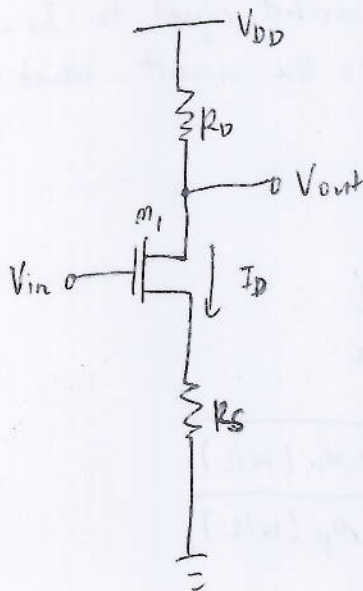

$$V_{out} = -I_D R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = - \left(\frac{\partial I_D}{\partial V_{in}} \right) R_D$$

$$\text{Let } G_m = \frac{\partial I_D}{\partial V_{in}},$$

$$\text{Assuming } I_D = f(V_{GS}),$$

$$G_m = \frac{\partial f}{\partial V_{GS}} \frac{\partial V_{GS}}{\partial V_{in}}$$

$$\text{Since } V_{GS} = V_{in} - I_D R_S,$$

$$\frac{\partial V_{GS}}{\partial V_{in}} = 1 - R_S \frac{\partial I_D}{\partial V_{in}}$$

$$\therefore G_m = \left(1 - R_S \frac{\partial I_D}{\partial V_{in}} \right) \frac{\partial f}{\partial V_{GS}}$$

$$= (1 - R_S G_m) g_m$$

$$= \frac{g_m}{1 + g_m R_S}$$

Small-signal voltage gain,

$$A_V = -G_m R_D$$


$$= - \frac{g_m R_D}{1 + g_m R_S}$$

$$\text{For } R_S \gg \frac{1}{g_m}$$

$$G_m \approx \frac{1}{R_S}$$

$$\text{i.e. } \Delta I_D \approx \Delta V_{in} R_S$$

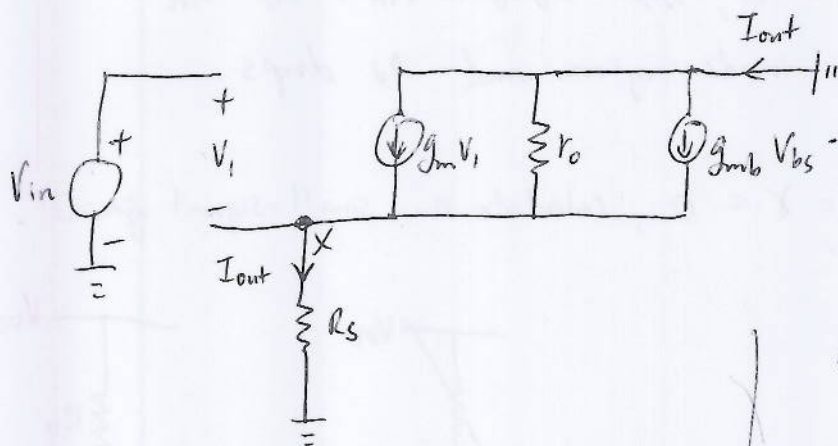Determine G_m in the presence of body effect and channel-length modulation.



$$V_{in} = V_1 + I_{out} R_S$$


Summing currents at node X,

$$I_{out} = g_m V_1 - g_{mb} V_{bs} - \frac{I_{out} R_S}{r_o}$$


$$= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_o}$$

$$G_m = \frac{I_{out}}{V_{in}}$$
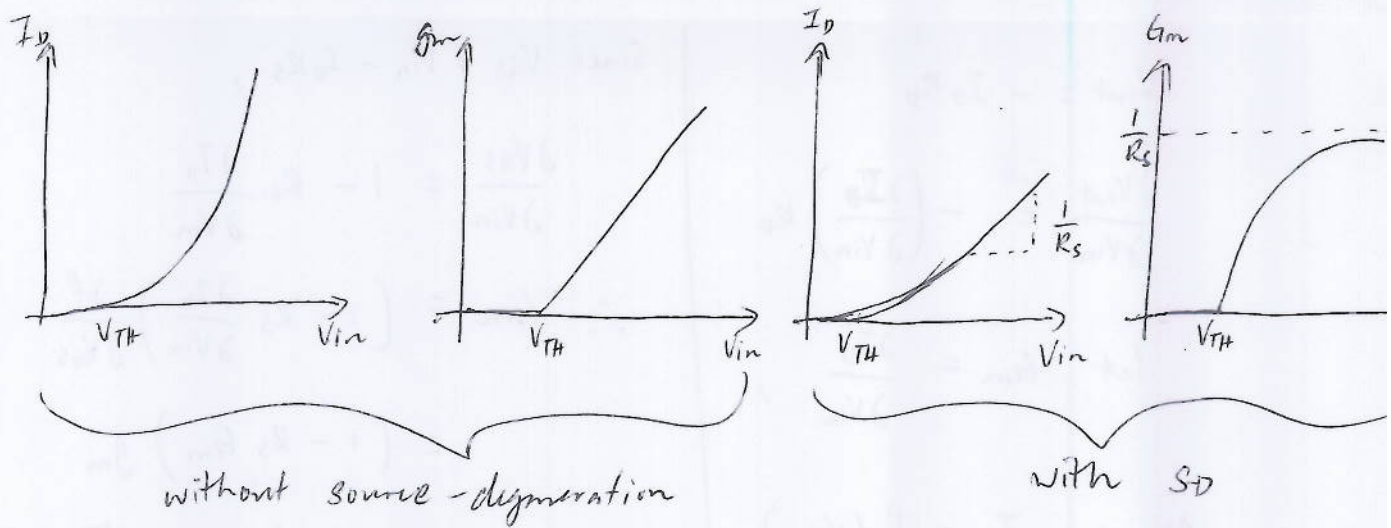
$$= \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$



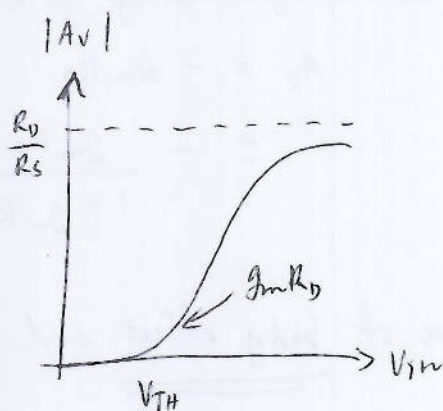(E.g.) Plot small-signal voltage gain as a function of the input bias voltage.




$$A_v = \frac{-g_m R_0}{1 + g_m R_s} = - \frac{R_0}{\frac{1}{g_m} + R_s}$$

For large values of V_{in} ,

$$g_m \approx \frac{1}{R_s} \therefore A_v = - \frac{R_0}{R_s}$$


If $V_{in} > V_{out} + V_{TH}$, ~~then~~ $R_0 I_D > V_{TH} + V_{DD} - V_{in}$
 M_1 enters the triode region and A_v drops.

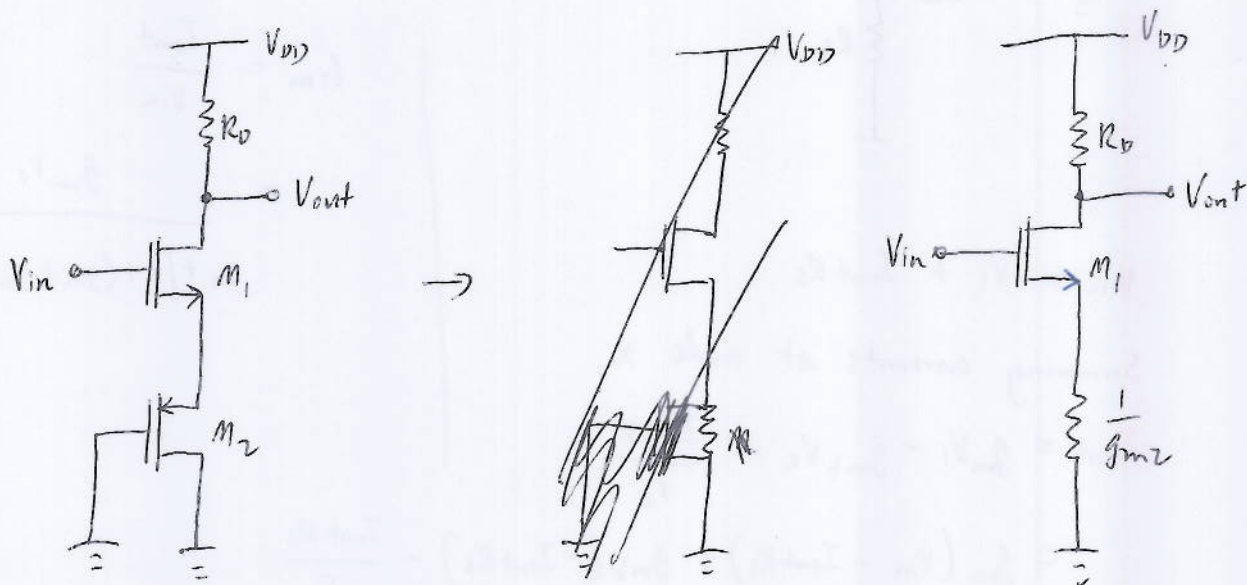(E.g.) Assuming $\lambda = \gamma = 0$, calculate the small-signal gain.



$$A_V = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

How to calculate output resistance?

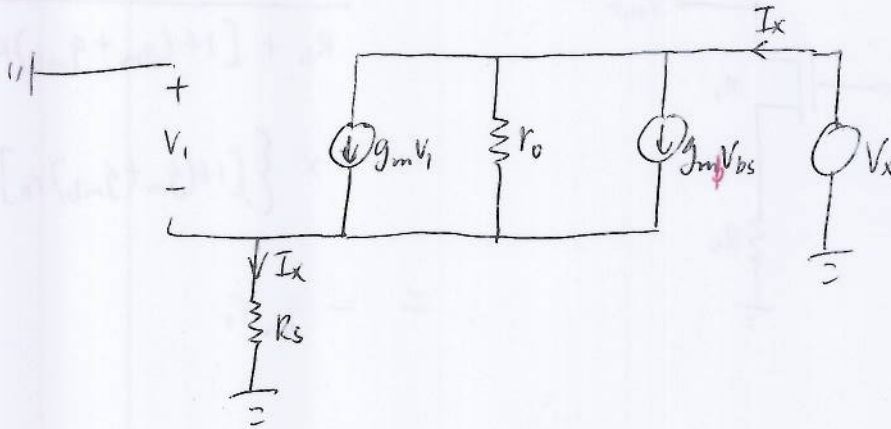

$$V_1 = -I_x R_s \Rightarrow$$

Current flowing through r_o , $I_x - (g_m + g_{mb}) V_1 = I_x + (g_m + g_{mb}) R_s I_x$

Adding voltage drop across r_o and R_s ,

$$r_o [I_x + (g_m + g_{mb}) R_s I_x] + I_x R_s = V_x$$

$$R_{out} = [1 + (g_m + g_{mb}) R_s] r_o + R_s$$

$$= [1 + (g_m + g_{mb}) r_o] R_s + r_o$$


since typically $(g_m + g_{mb}) r_o \gg 1$,

$$R_{out} \approx (g_m + g_{mb}) r_o R_s + r_o$$

$$= [1 + (g_m + g_{mb}) R_s] r_o$$

(Eg.)

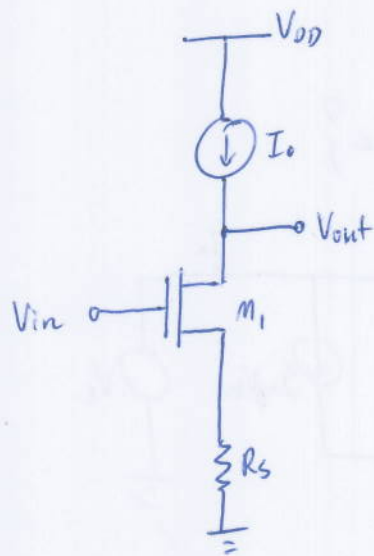Calculate the voltage gain of the circuit below. Assume I_0 is ideal.



$$A_v = G_m \times R_{out}$$

$$= - \frac{g_m r_o}{R_s + [1 + (g_m + g_{mb}) R_s] r_o}$$



$$\times \{ [1 + (g_m + g_{mb}) r_o] R_s + r_o \}$$

$$= - g_m r_o$$

- If I_0 is ideal, the current through R_s cannot change and hence the small-signal voltage drop across R_s is zero.

Source Follower (common-drain stage)

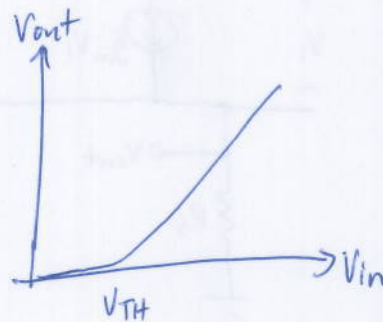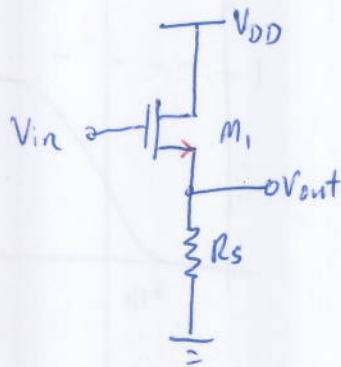- Common-source stage \rightarrow achieve high voltage gain with limited supply voltage, the load must be as large as possible.
- If such a stage is to drive a low-impedance load, then a "buffer" must be placed after the amplifier so as to drive the load with negligible loss of the signal level.



$V_{in} < V_{TH}$, M_1 is off, $V_{out} = 0$

$V_{in} > V_{TH}$, M_1 in saturation, I_{D1} flows through R_s .

$$I_{D1} R_s = V_{out}$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})^2 R_s = V_{out}$$

To calculate small-signal gain, differentiate both side with respect to V_{in} (include body effect)

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2 (V_{in} - V_{TH} - V_{out}) \left(1 - \frac{\partial V_{TH}}{\partial V_{in}} - \frac{\partial V_{out}}{\partial V_{in}} \right) R_s = \frac{\partial V_{out}}{\partial V_{in}}$$

$$\text{Since } \frac{\partial V_{TH}}{\partial V_{in}} = \eta \frac{\partial V_{out}}{\partial V_{in}}$$



$$\frac{\partial V_{out}}{\partial V_{in}} = \frac{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out}) R_s}{1 + \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out}) R_s (1 + \eta)}$$

Note that $g_m = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})$

$$\therefore A_v = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s}$$

Now prove using small-signal equivalent circuit,

$$\eta = \frac{g_{mb}}{g_m}$$

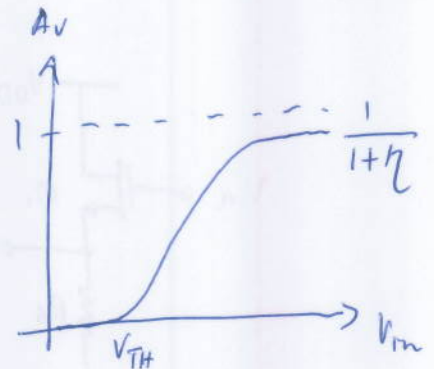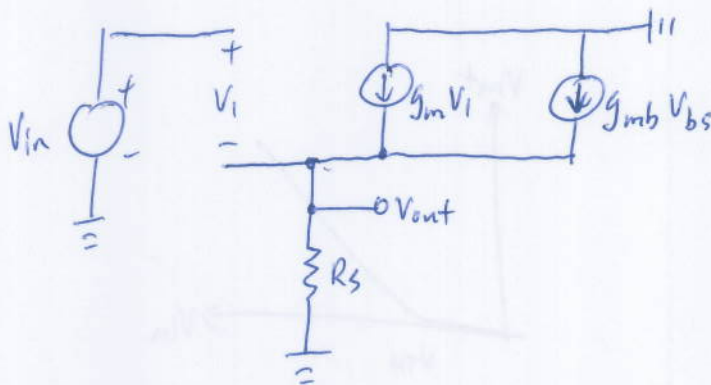

① $V_{in} = V_1 = V_{out}$, ② $V_{bs} = -V_{out}$, ③ $g_m V_1 - g_{mb} V_{out} = V_{out} / R_s$
 $V_1 = V_{out} - V_{in}$

$$A_v = \frac{V_{out}}{V_{in}} = g_m R_s / [1 + (g_m + g_{mb}) R_s]$$

$$\cancel{R_s g_m V_1} = \cancel{R_s g_{mb} V_{out}} + V_{out}$$



$$V_{out} = \frac{R_s g_m V_1}{R_s g_{mb} + 1}$$

If g_m increases ,

$$A_v = \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}$$

⊛ Even if $R_s = \infty$, the voltage gain of a source follower is not equal to one.

E.g.

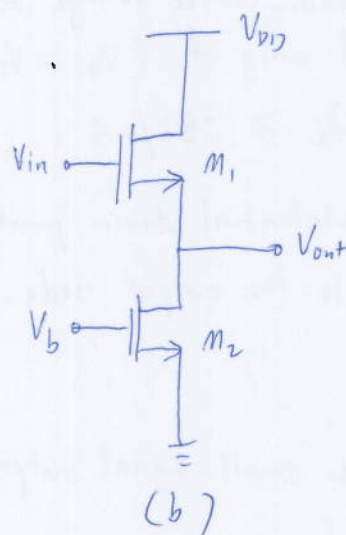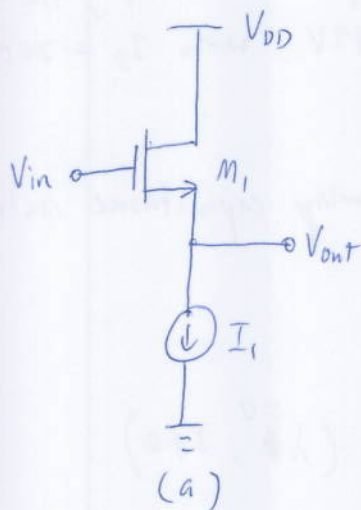

Suppose in the source follower of Fig(a) above, $(W/L)_1 = 20/0.5$, $I_1 = 200 \mu A$, $V_{TH0} = 0.6 V$, $2\phi_F = 0.7 V$, $\mu_n C_{ox} = 50 \mu A/V^2$ and $\gamma = 0.4 V^{1/2}$.

a) calculate V_{out} for $V_{in} = 1.2 V$.

b) If I_1 is implemented as M_2 in Fig. (b), find minimum value of $(W/L)_2$ for which M_2 remains saturated.

Solution

a) Since the threshold voltage of M_1 depends on V_{out} , we perform a simple iteration. Noting that

$$(V_{in} - V_{TH} - V_{out})^2 = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}$$

We first assume $V_{TH} \approx 0.6 V$, obtaining $V_{out} = 0.153 V$. Now we calculate a new V_{TH} as

$$V_{TH} = V_{TH0} + \gamma \left[\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right]$$

$$= 0.635 V$$

This indicates V_{out} is approximately 35mV less than that calculated above i.e. $V_{out} \approx 0.119 V$.


$$V_{TH0} = \Phi_{MS} + 2\phi_F + \frac{Q_{dep}}{C_{ox}}$$

Eg. $t_{ox} \approx 50 \text{ \AA}$
 $C_{ox} \approx 6.9 \text{ fF}/\mu m^2$

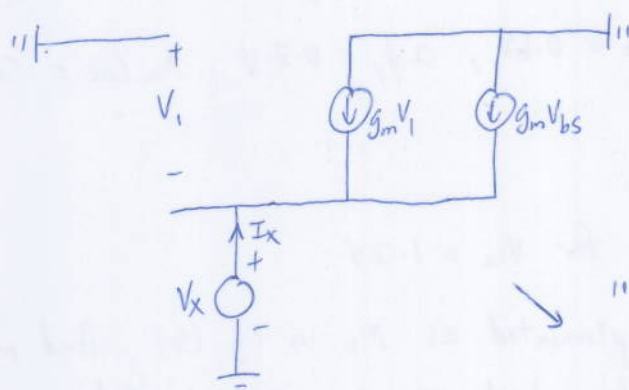- b) Since the drain-source voltage of M_2 is equal to $0.119V$, the device is saturated only if $(V_{as} - V_{TH})_2 \leq 0.119V$. With $I_D = 200\mu A$, this gives $(W/L)_2 \geq 283/0.5$.

(Note the substantial drain junction and overlap capacitance contributed by M_2 to the output node.)


(E.g.) Calculate small-signal output resistance. ($\lambda \stackrel{=}{\neq} 0$, $\gamma \neq 0$)



$$V_1 = -V_X$$



$$I_X - g_m V_X - g_{mb} V_X = 0$$
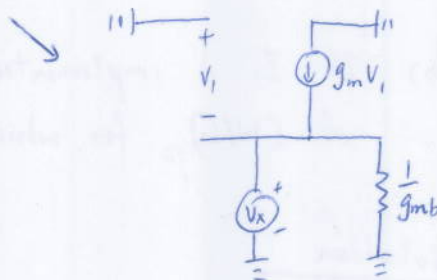
$$\therefore R_{out} = \frac{1}{g_m + g_{mb}}$$



(E.g.)


Find small-signal gain.

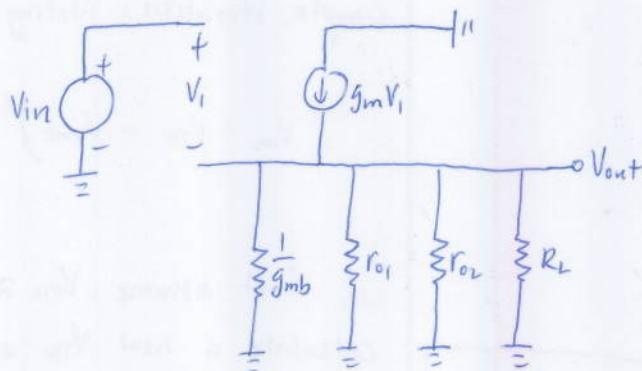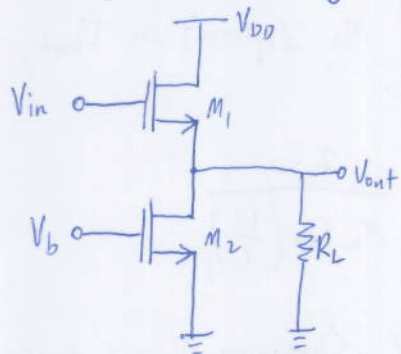

You can use simple voltage divider,


$$A_V = \frac{\frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2} \parallel R_L}{\frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2} \parallel R_L + \frac{1}{g_m}}$$

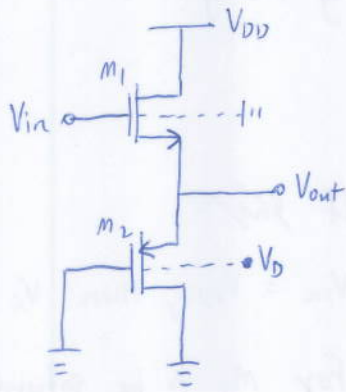(E.g.) Calculate voltage gain ($\gamma \neq 0, \lambda \neq 0$)



$$A_v = \frac{\frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}}}{\frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} + \frac{1}{g_{m1}}}$$

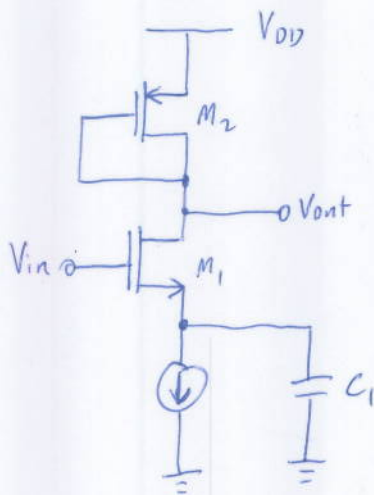(E.g.) a) Calculate the voltage gain if C_1 acts as an ac short at the frequency of interest. What is the maximum dc level of input signal for which M_1 remains saturated?




$$A_v = -g_{m1} [r_{o1} \parallel r_{o2} \parallel (1/g_{m2})]$$

Since $V_{out} = V_{DD} - |V_{ds2}|$, the maximum allowable dc level of V_{in} is equal to $V_{DD} - |V_{ds2}| + V_{TH1}$.

$$V_{out} \geq V_{in} - V_{TH1}$$

$$V_{DD} - |V_{ds2}| + V_{TH1} \geq V_{in}$$

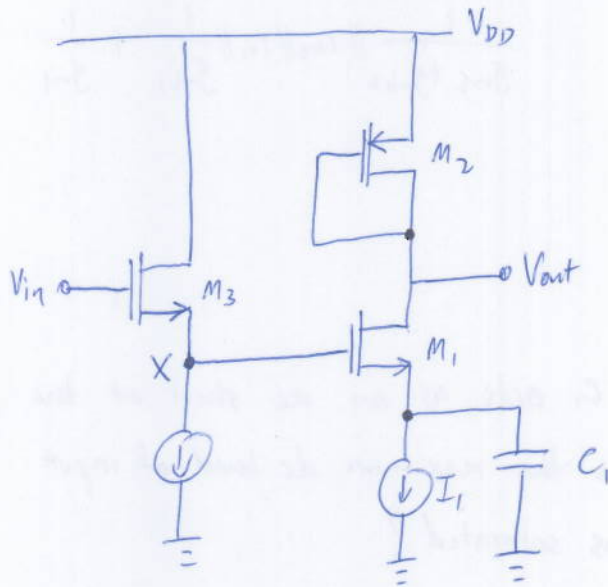- b) To accommodate an input level close to V_{DD} , the circuit is modified as shown in Fig. below. What relationship among the gate-source voltages of M_1 - M_3 guarantees that M_1 is saturated?



If $V_{out} =$

$$V_{in} = V_{DD}, \text{ then } V_X = V_{DD} - V_{GS3}.$$


For M_1 to be saturated,

$$V_{DD} - V_{GS3} - V_{TH1} \leq V_{DD} - |V_{GS2}|$$


$$\therefore V_{GS3} + V_{TH1} \geq |V_{GS2}|.$$

Common-Gate Stage

gives low input impedance

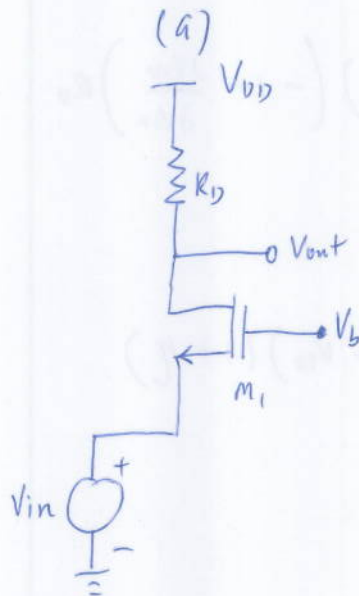

CG stage with direct coupling at input

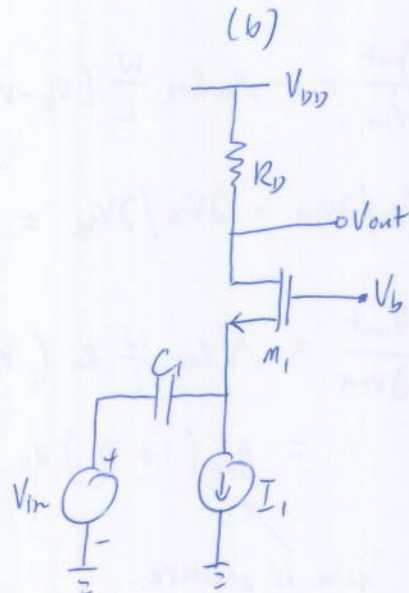

CG stage with capacitive coupling at input.

First study large-signal behaviour for (a),

For simplicity assume that V_{in} decreases from large positive value.

$$V_{in} \geq V_b - V_{TH}, M_1 \text{ is off}$$

$$\therefore V_{out} = V_{DD}$$

For lower values of V_{in} ,


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2, \text{ if } M_1 \text{ is in saturation.}$$

As V_{in} decreases, so does V_{out} , eventually drive M_1 into triode region if

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D = V_b - V_{TH}$$

Input-output characteristic if M_1 in saturation,
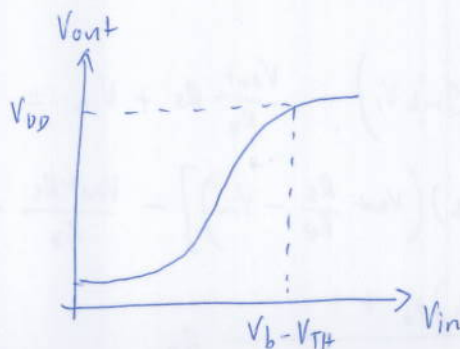
$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$



Small-signal gain ?



$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D$$

Since $\frac{\partial V_{TH}}{\partial V_{in}} = \frac{\partial V_{TH}}{\partial V_{SB}} = \eta$,

$$\begin{aligned} \frac{\partial V_{out}}{\partial V_{in}} &= \mu_n C_{ox} \frac{W}{L} R_D (V_b - V_{in} - V_{TH}) (1 + \eta) \\ &= g_m (1 + \eta) R_D \end{aligned}$$

gain is positive.

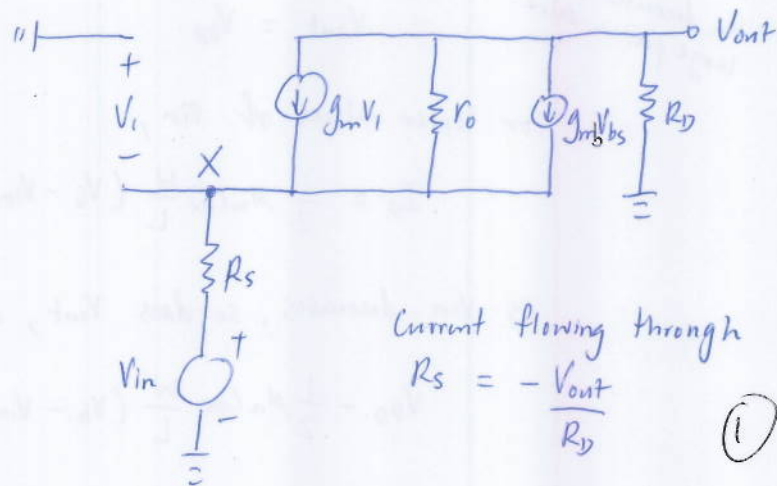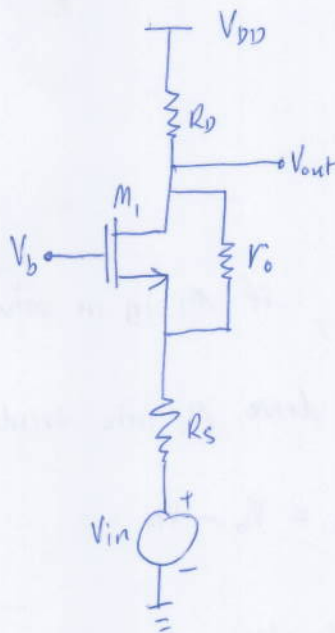Now study CG stage taking into account both output impedance of the transistor and the impedance of the signal source. ($\lambda \neq 0, \gamma \neq 0$)



Current flowing through

$$R_S = -\frac{V_{out}}{R_D} \quad (1)$$

$$V_i - \frac{V_{out}}{R_D} R_S + V_{in} = 0 \quad (2)$$

$$I_{r_0} = -\frac{V_{out}}{R_D} - g_m V_i - g_{mb} V_i$$


$$r_0 \left(-\frac{V_{out}}{R_D} - g_m V_i - g_{mb} V_i \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out} \quad (3)$$

$$\therefore r_0 \left[-\frac{V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \frac{R_S}{R_D} - V_{in} \right) \right] - \frac{V_{out} R_S}{R_D} + V_{in} = V_{out}$$

$$\Rightarrow \therefore \frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb}) r_0 + 1}{r_0 + (g_m + g_{mb}) r_0 R_S + R_S + R_D} R_D$$

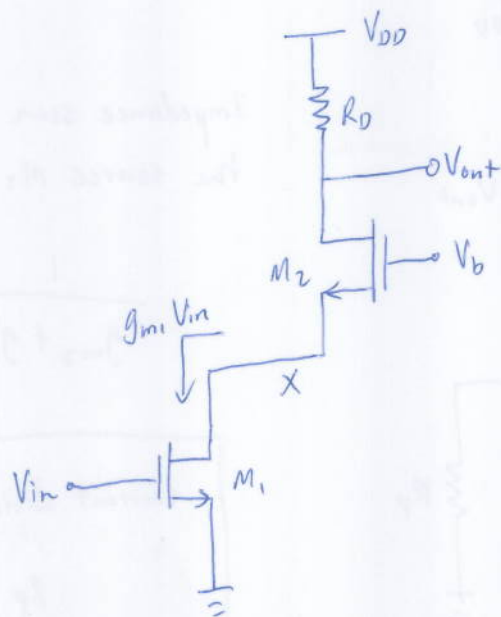(2)

Cascode Stage (cascade of a CS stage and a CG stage)




M_1 = input device
 M_2 = cascode device


$$M_1 \text{ sat, } V_X \geq V_{in} - V_{TH1}$$

$$M_1, M_2 \text{ sat, } V_X = V_b - V_{GS2}$$
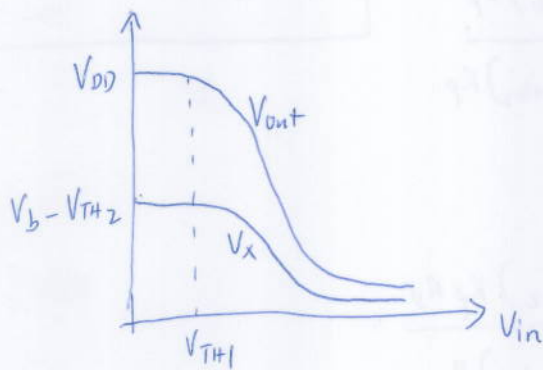
$$M_2 \text{ sat, } V_{out} \geq V_b - V_{TH2}$$




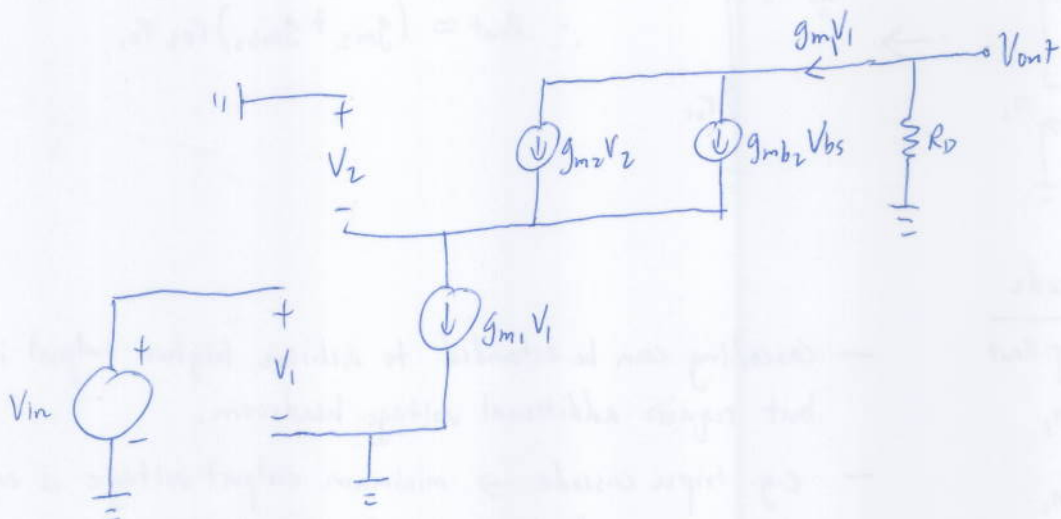Small-signal equivalent circuit $\lambda = 0, \gamma \neq 0$



(E.g.)

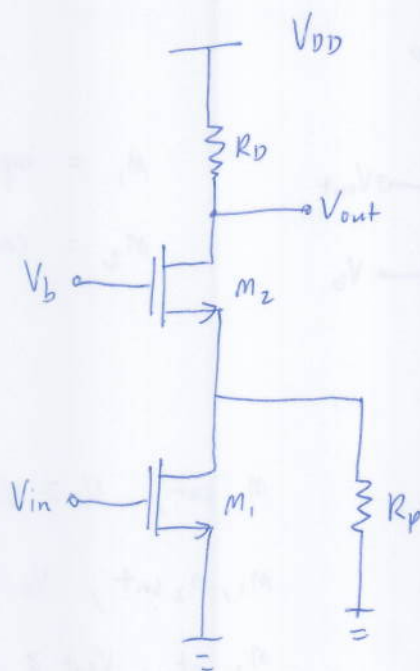Calculate voltage gain if $\lambda = 0$, $r \neq 0$



Impedance seen looking into the source M_2 ,

$$\frac{1}{g_{m2} + g_{mb2}}$$



Current divider rule:

$$\frac{R_p}{\frac{1}{g_{m2} + g_{mb2}} + R_p} g_{m1} V_{in}$$

$$I_{D2} = g_{m1} V_{in} \frac{(g_{m2} + g_{mb2}) R_p}{1 + (g_{m2} + g_{mb2}) R_p}$$

Voltage gain,
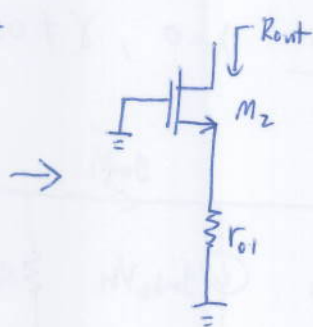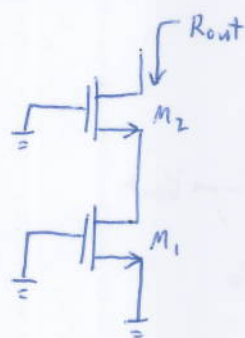
$$A_v = - \frac{g_{m1} (g_{m2} + g_{mb2}) R_p R_D}{1 + (g_{m2} + g_{mb2}) R_p}$$




Same as R_{out} for common-source stage with r_{o1} degeneration

$$R_{out} = [1 + (g_{m2} + g_{mb2}) r_{o2}] r_{o1} + r_{o2}$$

$$\therefore R_{out} \approx (g_{m2} + g_{mb2}) r_{o2} r_{o1}$$


Triple cascode

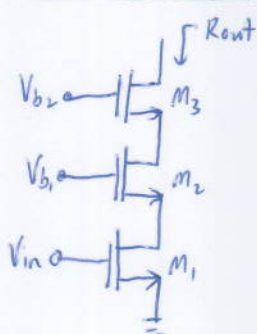


— cascoding can be extended to achieve higher output impedance but require additional voltage headroom.

— e.g. triple cascode \rightarrow minimum output voltage is equal to the sum of three overdrive voltages.


Folded cascode (Pmos - Nmos)

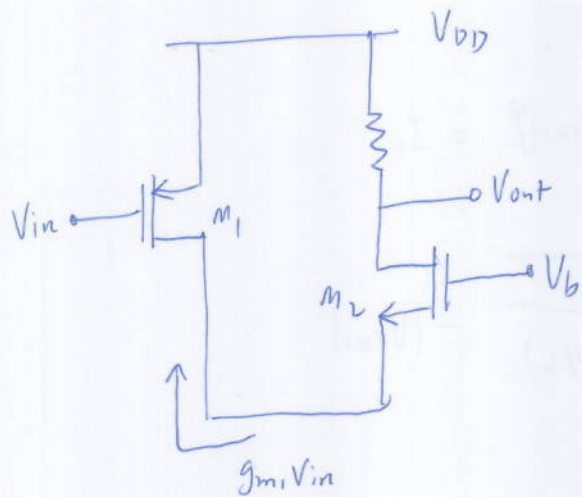



(a) simple

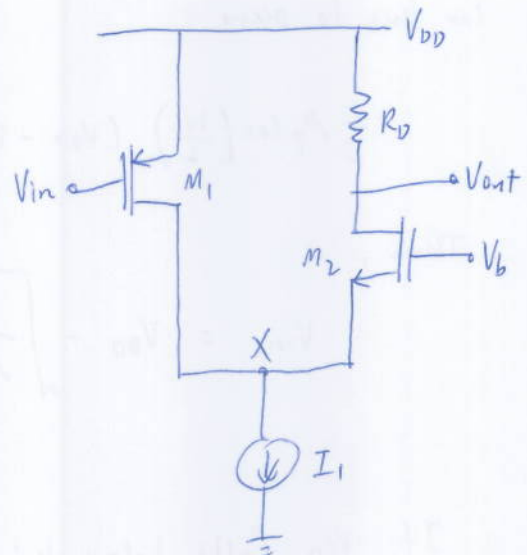

(b) with proper biasing

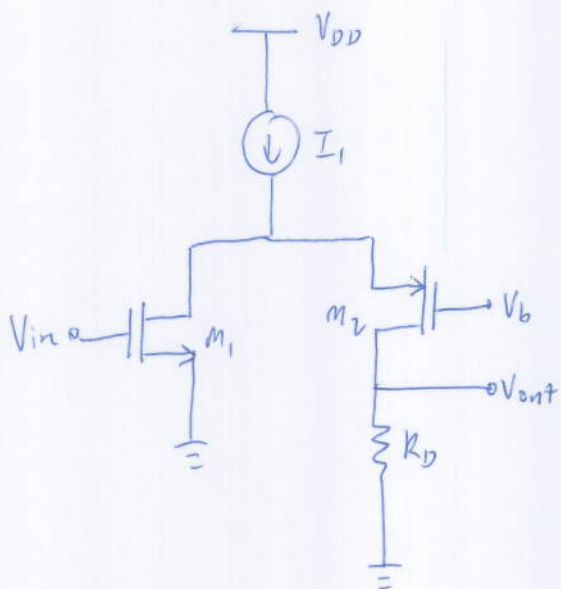

(c) with Nmos input

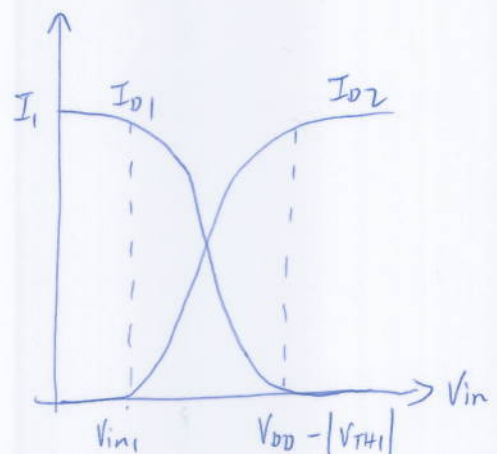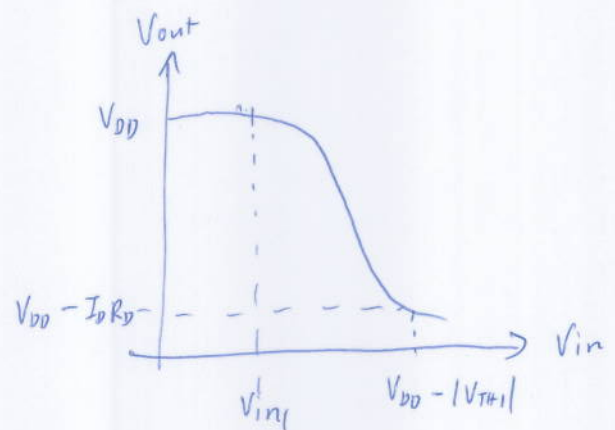

(b) $V_{in} > V_{DD} - |V_{TH1}|$, M_1 is off and M_2 carries all of I_1 .

$$\therefore V_{out} = V_{DD} - I_1 R_D$$

$V_{in} < V_{DD} - |V_{TH1}|$, M_1 is on in saturation.

$$I_{D2} = I_1 - \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{in} - |V_{TH1}|)^2$$

As V_{in} drops, I_{D2} decreases further, falling to zero if $I_{D1} = I_1$.

For this to occur:

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{in1} - |V_{TH1}|)^2 = I_1$$

Thus,

$$V_{in1} = V_{DD} - \sqrt{\frac{2I_1}{\mu_p C_{ox} (W/L)_1}} - |V_{TH1}|$$

If V_{in} falls below this level, I_{D1} tends to be greater than I_1 and M_1 enters the triode region so as to allow $I_{D1} = I_1$.