
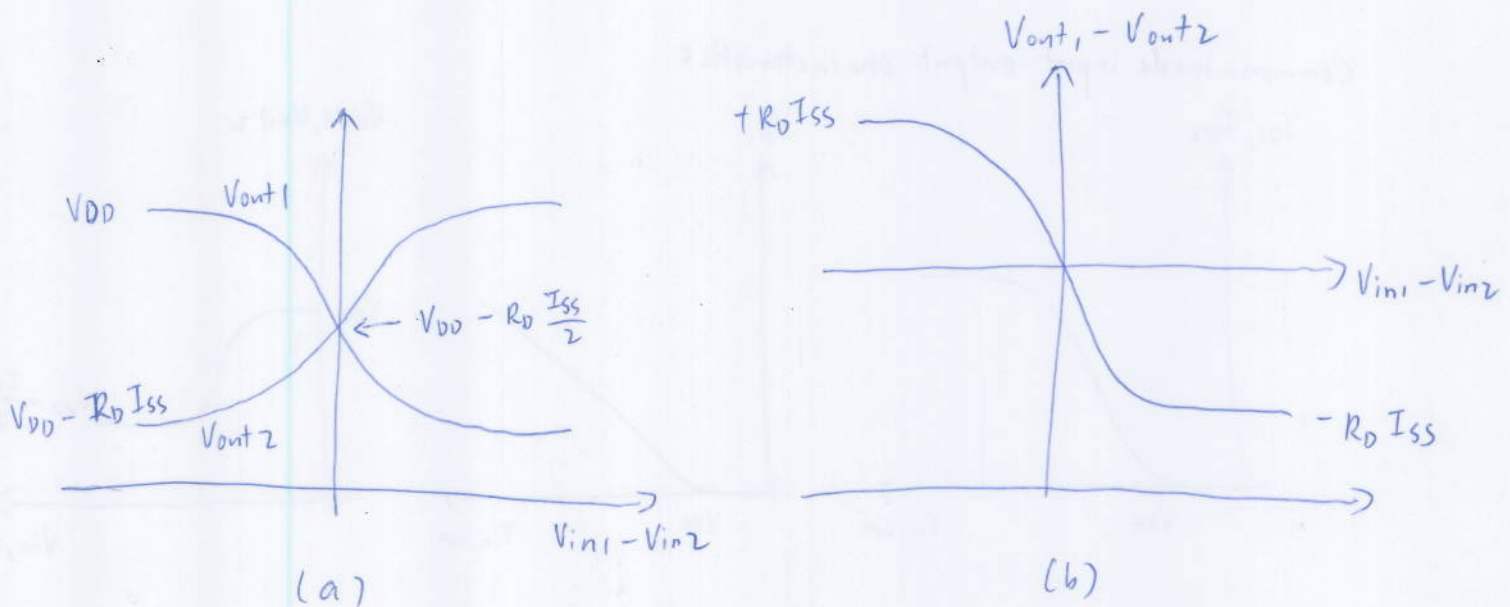


## Basic differential pair

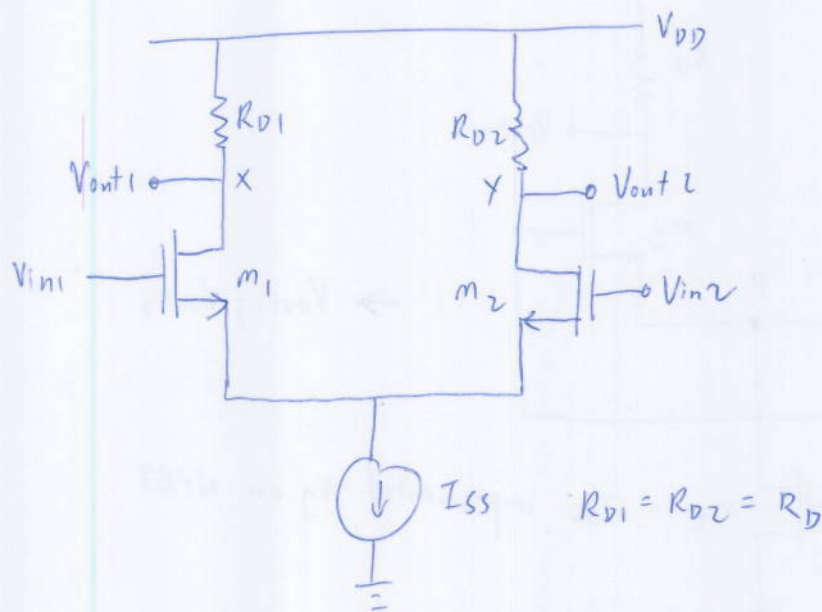

Input - Output Characteristics.


For  $\Delta V_{in} = 0$ ,  $G_m = \sqrt{\mu_n C_{ox} (W/L) I_{ss}}$

$V_{out1} - V_{out2} = R_D \Delta I = R_D G_m \Delta V_{in}$ ,

Small-signal differential voltage gain

$$|A_v| = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{ss}} \cdot R_D$$
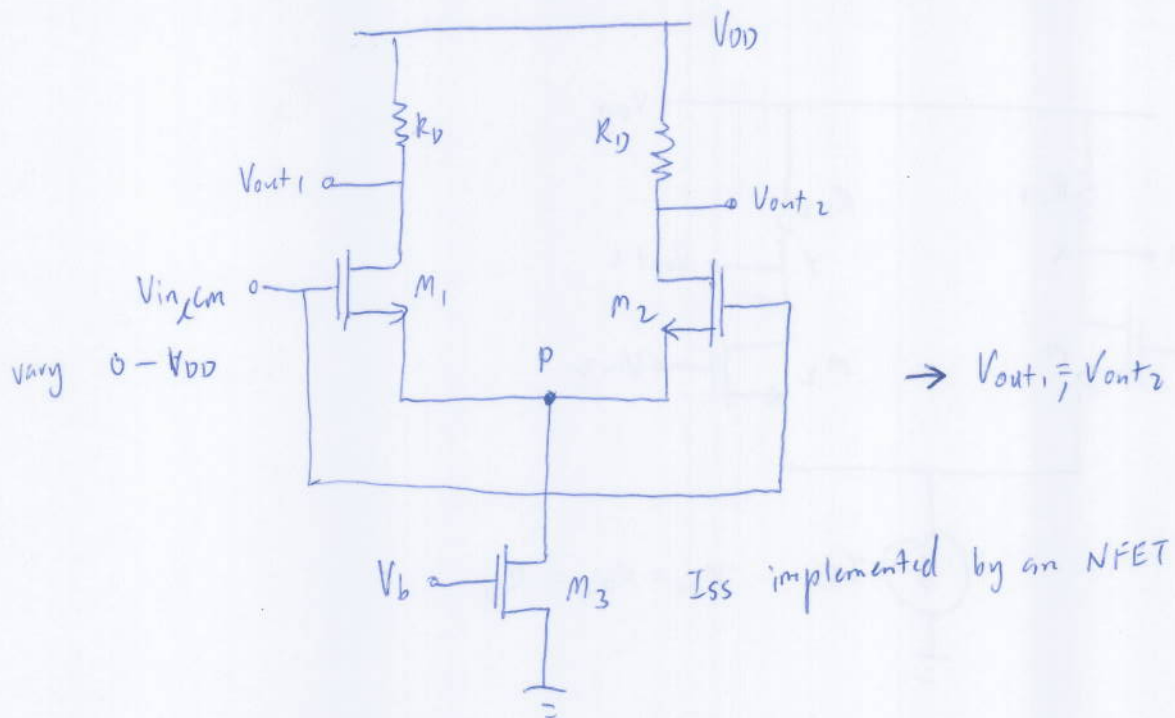
## Differential pair sensing an input common-mode change



Common-mode input-output characteristics.




Proper operation  $V_{in,cm} \geq V_{GS1} + (V_{GS3} - V_{TH3})$

$M_1$  and  $M_2$  enter triode region  $V_{in,cm} > V_{out1} + V_{TH} = V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}$

Allowable values of  $V_{in,cm}$  is bounded as follows:
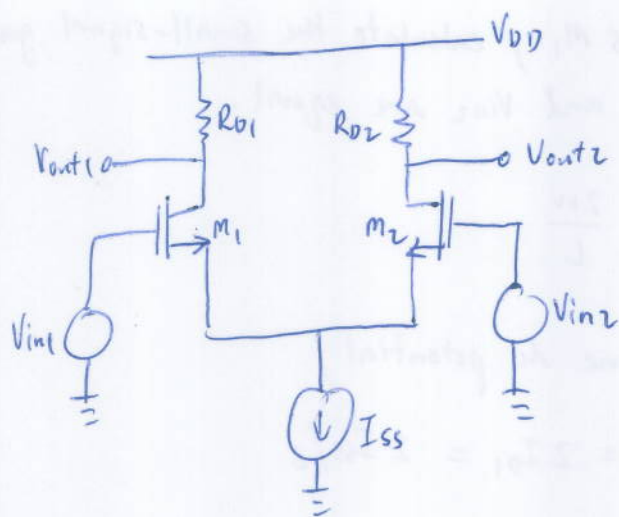
$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,cm} \leq \min \left[ V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$



Differential gain?

$$\lambda = \gamma = 0$$

$$R_{01} = R_{02} = R_D$$

Superposition:

$$\frac{V_x}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

← acting like common-source

$$\frac{V_y}{V_{in2}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

← acting like common-gate

∴ Overall gain due to  $V_{in1}$ ,  $V_x - V_y = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$

if  $g_{m1} = g_{m2} = g_m$ ,

$$(V_x - V_y)|_{\text{due to } V_{in1}} = -g_m R_D V_{in1}$$

$$(V_x - V_y)|_{\text{due to } V_{in2}} = +g_m R_D V_{in2}$$

∴  $\frac{(V_x - V_y)_{\text{total}}}{V_{in1} - V_{in2}} = -g_m R_D$

(E.g.)

If  $m_2$  is twice as wide as  $m_1$ , calculate the small-signal gain if the bias values of  $V_{in1}$  and  $V_{in2}$  are equal.

$$m_1 : \frac{W}{L} \quad m_2 : \frac{2W}{L}$$

$m_1$  and  $m_2$  gates at same dc potential,

$$V_{GS1} = V_{GS2} \quad \text{and} \quad I_{D2} = 2I_{D1} = 2I_{SS}/3$$

$$\therefore g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} \cdot \frac{I_{SS}}{3}} \quad , \quad g_{m2} = \sqrt{2\mu_n C_{ox} \left(\frac{2W}{L}\right) \frac{2I_{SS}}{3}} = 2g_{m1}$$


$$|A_v| = \frac{2R_D}{\frac{1}{g_{m1}} + \frac{1}{2g_{m1}}} = \frac{4}{3} g_{m1} R_D$$

[Note that this value is lower than the gain of a symmetric differential pair (with  $2W/L$  for each device)]
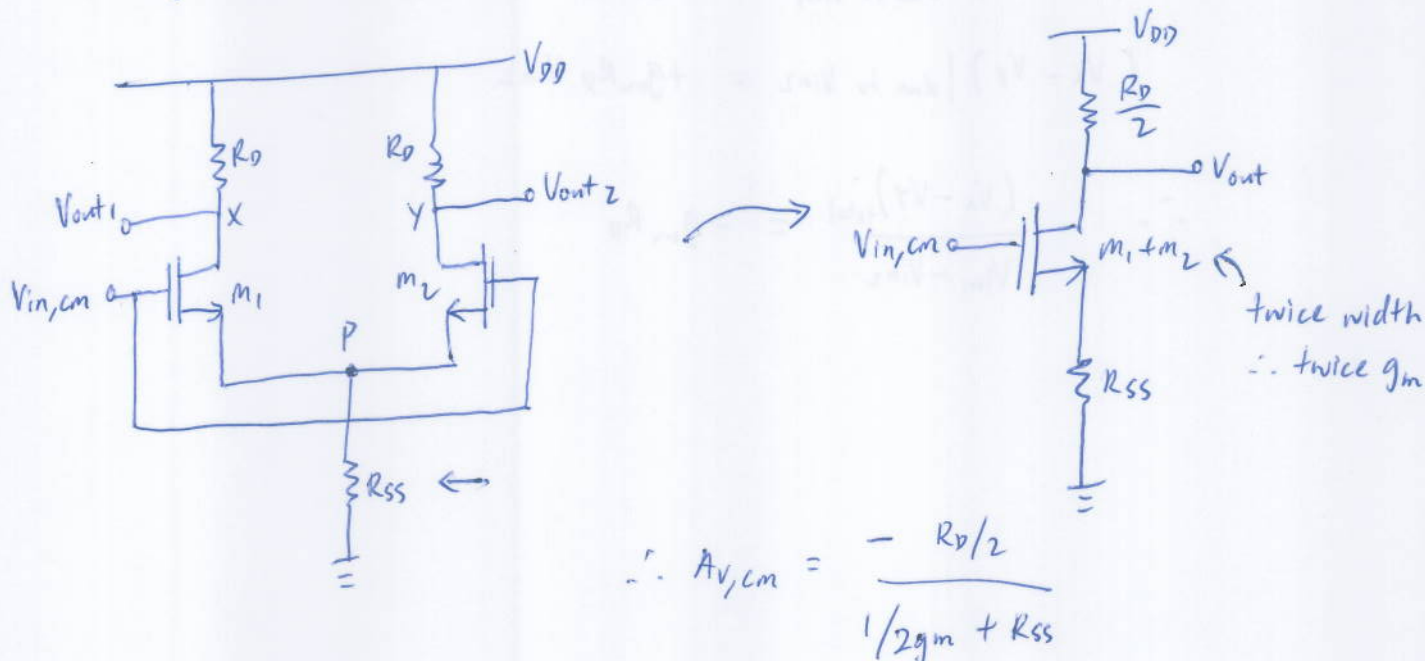
### Common-mode Response


- circuit not fully symmetric in reality
- current source not infinite output impedance } fraction of CM variation appears at the output.

If symmetric but <sup>current source has a</sup> finite output impedance  $R_{SS}$





(E.g.)

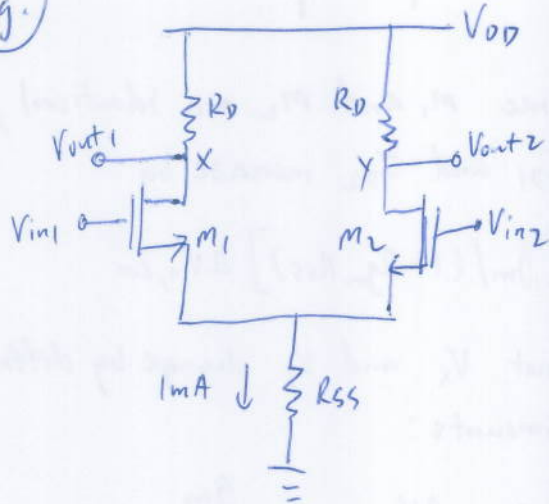

Assume  $(W/L)_{1,2} = 25/0.5$

$\mu_n C_{ox} = 50 \mu A/V^2$

$V_{TH} = 0.6 V$

$\lambda = \gamma = 0$

$V_{DD} = 3 V$

a) What is the required input CM for which  $R_{ss}$  sustains 0.5V?

Since  $I_{D1} = I_{D2} = 0.5 mA$ ,

$$V_{GS1} = V_{GS2} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

$$= 1.23 V$$

$R_{ss} = 500 \Omega$

$\therefore V_{in,cm} = V_{GS1} + 0.5V = 1.73V //$

b) Calculate  $R_D$  for a differential gain of 5.

The transconductance of each device is  $g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_{D1}}$

$|A_v| = g_m R_D$

$= \frac{1}{632 \Omega}$

requiring  $R_D = 3.16 k\Omega //$

c) What happens at the output if the input CM level is 50mV higher than the value calculated in (a)?


$$|4 V_{x,y}| = \Delta V_{in,cm} \frac{R_D/2}{R_{ss} + 1/(2g_m)}$$

$= 50mV \times 1.94$

$= 96.8 mV.$

Now  $m_1$  and  $m_2$  are only 143mV away from the triode region because the input CM level has increased by 50mV and the output CM level has decreased by 96.8mV.

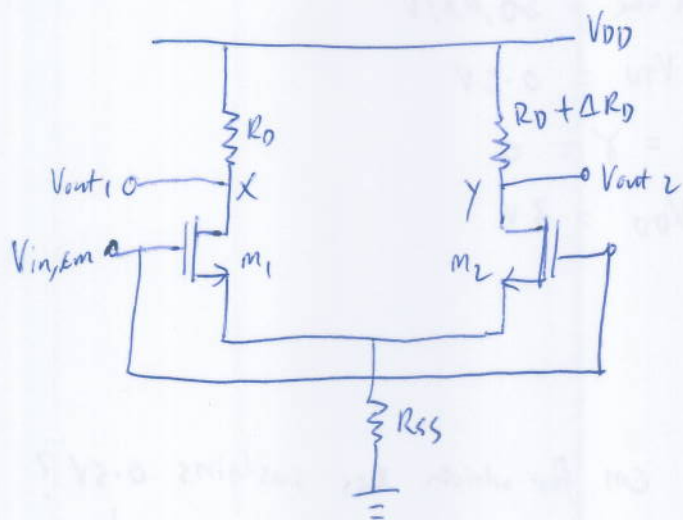Now consider non-symmetric and finite output impedance  
asymmetry



Resistor mismatch:

Since  $m_1$  and  $m_2$  are identical,  
 $I_{D1}$  and  $I_{D2}$  increase by

$$\left[ \frac{g_m}{1 + 2g_m R_{ss}} \right] \Delta V_{in,cm}$$

but  $V_x$  and  $V_y$  change by different amounts:

$$\Delta V_x = - \Delta V_{in,cm} \frac{g_m}{1 + 2g_m R_{ss}} R_0$$

$$\Delta V_y = - \Delta V_{in,cm} \frac{g_m}{1 + 2g_m R_{ss}} (R_0 + \Delta R_0)$$

— common-mode change at the input introduces a differential component at the output.

If  $m_1$  and  $m_2$  mismatch? (threshold voltage mismatch)

$$I_{D1} = g_{m1} (V_{in,cm} - V_p)$$

$$I_{D2} = g_{m2} (V_{in,cm} - V_p)$$

$$(g_{m1} + g_{m2})(V_{in,cm} - V_p) R_{ss} = V_p$$

$$V_p = \frac{(g_{m1} + g_{m2}) R_{ss}}{(g_{m1} + g_{m2}) R_{ss} + 1} V_{in,cm}$$

Output voltages ,

$$V_x = -g_{m1} (V_{in,cm} - V_p) R_0$$

$$= \frac{-g_{m1}}{(g_{m1} + g_{m2}) R_{ss} + 1} R_0 V_{in,cm}$$

and

$$V_y = -g_{m2} (V_{in,cm} - V_p) R_0$$

$$= \frac{-g_{m2}}{(g_{m1} + g_{m2}) R_{ss} + 1} R_0 V_{in,cm}$$

$$V_x - V_y = \frac{-(g_{m1} - g_{m2})}{(g_{m1} + g_{m2}) R_{ss} + 1} R_0 V_{in,cm}$$

$$\therefore A_{cm-dm} = \frac{4g_m R_0}{(g_{m1} + g_{m2}) R_{ss} + 1}$$

$A_{cm-dm} \rightarrow$  common-mode to differential-mode conversion

$$\Delta g_m = g_{m1} - g_{m2}$$

For meaningful comparison of differential circuits, the undesirable differential component produced by CM variations must be normalised to the wanted differential output resulting from amplification.

Common-mode rejection ratio (CMRR),

$$CMRR = \left| \frac{A_{dm}}{A_{cm-dm}} \right|$$

If only  $g_m$  mismatch is considered, we can show

$$|A_{dm}| = \frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}}$$


where it is assumed  $V_{in1} = -V_{in2}$  and hence

$$\begin{aligned} CMRR &= \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m} \\ &\approx \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS}) \end{aligned}$$

where  $g_m$  denotes the mean value, i.e.  $g_m = (g_{m1} + g_{m2})/2$




## Differential Pair with MOS Loads

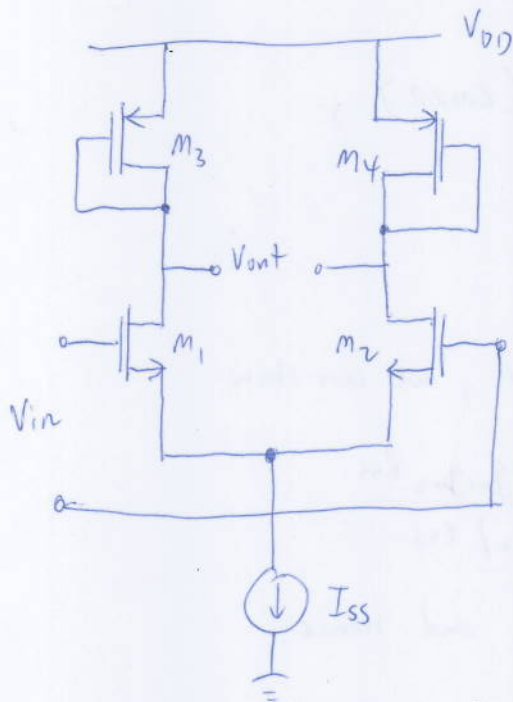

$$A_V = -g_{mN} (g_{mp}^{-1} \parallel r_{oN} \parallel r_{oP})$$

$$\approx -\frac{g_{mN}}{g_{mP}}$$
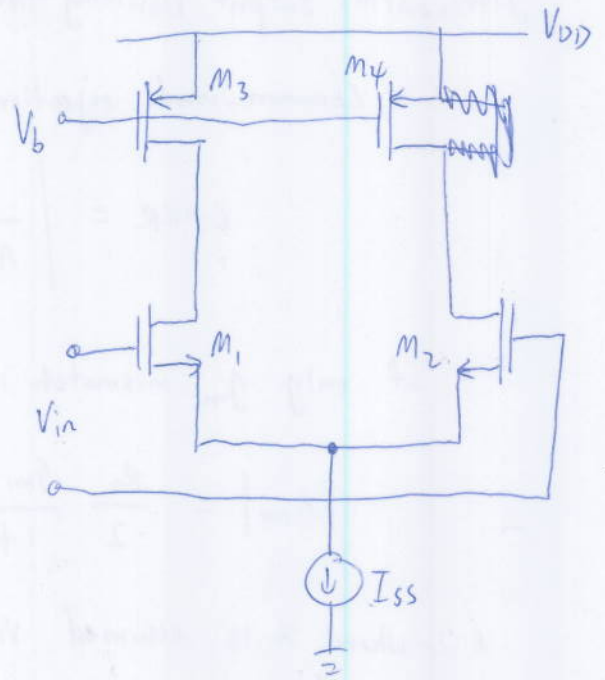
$$\therefore \approx -\sqrt{\frac{\mu_n (W/L)_N}{\mu_p (W/L)_P}}$$



$$A_V = -g_{mN} (r_{oN} \parallel r_{oP})$$

- consumes voltage headroom
- trade-off between the output swings, voltage gain and input CM range.